 


# Lab01

## Experiment 1:

- 1 Design and verify a binary-to-Gray-code converter for a Gray code sequence with 10 code words (input:  $abcd$ , output:  $wxyz$ ,  $a$  and  $w$  are the MSB).
  - 1.1 Derive the Boolean function/logic equation.
  - 1.2 Draw the related logic diagram.
  - 1.3 Construct the Verilog RTL code for the converter and use a testbench to simulate the logic behavior for verification.


## Result:



## Experiment 2:

- 2 Design a signed 4-bit binary adder/subtractor with input  $a$  ( $a_3a_2a_1a_0$ ),  $b$  ( $b_3b_2b_1b_0$ ),  $m$  as the operator control (0 for addition and 1 for subtraction); output  $s$  ( $s_3s_2s_1s_0$ ),  $v$  as overflow indicator.
  - 2.1 Derive the Boolean function/logic equation.
  - 2.2 Draw the related logic diagram.
  - 2.3 Construct the Verilog RTL code for the function and use a given testbench to simulate the logic behavior for verification.

## Result:

 

## Experiment 3:

- 3 (Bonus) For three 3-bit signed numbers  $a$  ( $a_2a_1a_0$ ),  $b$  ( $b_2b_1b_0$ ), and  $c$  ( $c_2c_1c_0$ ), build a logic circuit to output  $o$  ( $o_2o_1o_0$ ) as the smallest number and use a given testbench for verification.

## Result:

