 


Lab01

Experiment 1:

- 1 Design and verify a binary-to-Gray-code converter for a Gray code sequence with 10 code words (input: $abcd$, output: $wxyz$, a and w are the MSB).
 - 1.1 Derive the Boolean function/logic equation.
 - 1.2 Draw the related logic diagram.
 - 1.3 Construct the Verilog RTL code for the converter and use a testbench to simulate the logic behavior for verification.

Result:




Binary	Gray
0000	0000
0001	0001
0010	0011
0011	0111
0100	0110
0101	1110
0110	1010
0111	1011
1000	1001
1001	1000

$$z = a\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}d + \bar{a}\bar{b}c + \bar{a}cd$$

$$y = \bar{a}c + \bar{a}b$$

$$x = \bar{a}\bar{b}cd + \bar{a}b\bar{c}$$

$$w = \bar{a}b\bar{c} + \bar{a}bd + \bar{a}bc$$

 

Experiment 2:

- 2 Design a signed 4-bit binary adder/subtractor with input a ($a_3a_2a_1a_0$), b ($b_3b_2b_1b_0$), m as the operator control (0 for addition and 1 for subtraction); output s ($s_3s_2s_1s_0$), v as overflow indicator.
 - 2.1 Derive the Boolean function/logic equation.
 - 2.2 Draw the related logic diagram.
 - 2.3 Construct the Verilog RTL code for the function and use a given testbench to simulate the logic behavior for verification.

Result:

Full adder:

$$\{c[1], s[0]\} = a[0] + (m \wedge b[0]) + m$$


$$\{c[2], s[1]\} = a[1] + (m \wedge b[1]) + c[1]$$

$$\{c[3], s[2]\} = a[2] + (m \wedge b[2]) + c[2]$$

$$\{c[4], s[3]\} = a[3] + (m \wedge b[3]) + c[3]$$

XOR:

$$v = c[3] \wedge c[4]$$

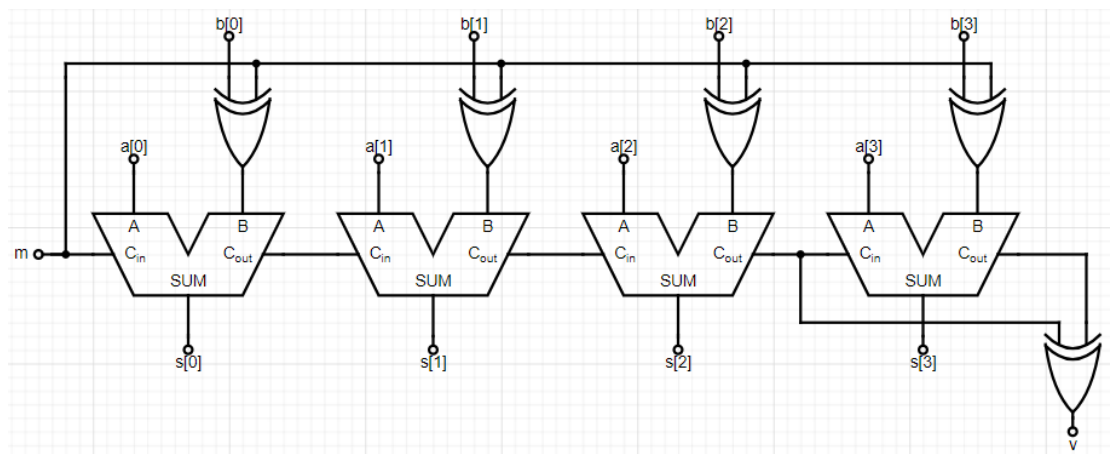

> a[3:0]	2	5	-3	-6	5
> b[3:0]	5	4	6	-7	-5
m	0				
> s[3:0]	7	-3	-7	7	3
v	0				

Experiment 3:

- 3 (Bonus) For three 3-bit signed numbers a ($a_2a_1a_0$), b ($b_2b_1b_0$), and c ($c_2c_1c_0$), build a logic circuit to output o ($o_2o_1o_0$) as the smallest number and use a given testbench for verification.

Result:

> a[2:0]	2	2	2	2	-2
> b[2:0]	3	-1	3	-1	3
> c[2:0]	1		-3		1
> o[2:0]	1	-3	-1	-2	